

University of Engineering & Technology, Peshawar

Programme: BSc Computer Systems Engineering

Semester: 3rd Semester

Paper: Digital Logic Design

Date: 10th March, 2021

Exam Type: Final Term

Allowed Time: 180 Minutes	Max Marks: 50
Student's Name:	
Student's Registration:	

Instructions:

- 1- This exam is OPEN books/notes/Internet.
- 2- Sharing of books, notes and other materials during this exam is not permitted.
- 3- Answer ALL questions on the question sheet.
- 4- There are 3 problems (and 9 questions) in total. Some questions are harder than others. Answer the easy ones first to maximize your score.
- 5- Questions will not be interpreted during the exam.

Problem 1: Decoders and Encoders (20 pts.)

1(a) (6 pts.)

The truth table shown below is for a 3-line to 8-line binary Decoder circuit:

Inputs			Outputs							
C	B	A	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

For each of the eight output lines, there is a Boolean expression describing its function. Write the Boolean expressions for output lines D₂, D₆, and D₇.

Solution:

D₂ = _____

D₆ = _____

D₇ = _____

1(b) (6 pts.)

Design a combinational circuit using a Decoder and OR gates. The circuit accepts a 2-bit number and generates an output binary number equal to the square of the input number.

Solution:

Truth Table:

Design:

1(c) (5 pts.)
Construct a 4x16 Decoder using 2x4 Decoders.

Solution:

1(d) (3 pts.)
What is a priority Encoder, and how does it differ from a regular Encoder?

Solution:

Problem 2: Multiplexers and De-Multiplexers (15 pts.)

2(a) (5 pts.)

Construct an 8x1 Multiplexer using two 4x1 Multiplexers and a 2x1 Multiplexer.

Solution:

2(b) (5 pts.)

Implement the following function using a Multiplexer.

$$F(A, B, C) = \sum_m (1, 4, 6, 7)$$

Solution:

2(c) (5 pts.)

Design a 1x4 De-Multiplexer using gates. Draw its truth table and logic circuit.

Solution:

Truth Table:

Logic Circuit:

Problem 3: Latches and Flip-Flops (15 pts.)

3(a) (5 pts.)

What is the difference between a Latch and a Flip-Flop?

Solution:

3(b) (10 pts.)

The waveforms in Fig 1 are applied to the J, K and CLK inputs of the positive edge-triggered JK flip-flop shown in Fig 2. Determine the Q output, starting in RESET state.

 


Fig 1. Input waveforms

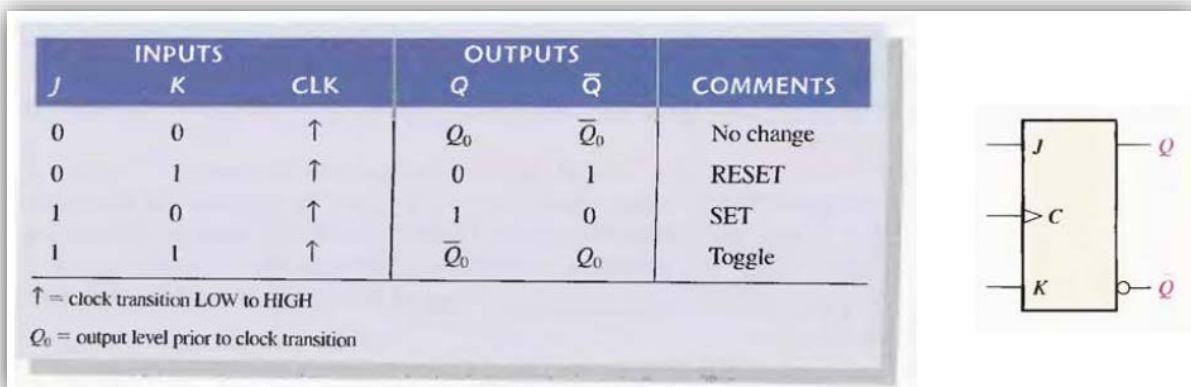


Fig 2. Truth table (left) and logic symbol (right) for a positive edge-triggered JK flip-flop

Solution: