

Circuits and Systems 1 - Last Week Lecture

Problem 7.2-2 on page 294

If the capacitance of a capacitor is equal to $C = 0.125F$ and voltage across capacitor is $v(t) = 12 \cos(2t + 30^\circ)V$, then compute the current across the capacitor?

Solution: The formula for computing current is as follows:

$$i = C \frac{dv}{dt}$$

Also, the following formula is stated:

$$\frac{d}{dt} A \cos(\omega t + \theta) = A\omega \cos(\omega t + (\theta + \frac{\pi}{2}))$$

Problem 7.2-2 on page 294

Let us first compute $\frac{dv}{dt}$ as follows:

$$\begin{aligned}\frac{d}{dt} A \cos(\omega t + \theta) &= A \omega \cos\left(\omega t + \left(\theta + \frac{\pi}{2}\right)\right) \\ \frac{d}{dt} 12 \cos(2t + 30^\circ) &= 12(2) \cos\left(2t + \left(30^\circ + \frac{\pi}{2}\right)\right) \\ &= 24 \cos(2t + 120^\circ)\end{aligned}$$

When we plug-in the values, the following is obtained:

$$\begin{aligned}i &= C \frac{dv}{dt} \\ &= 0.125 \times 24 \cos(2t + 120^\circ) \\ &= 3 \cos(2t + 120^\circ)\end{aligned}$$

Problem 7.2-3 on page 295

Determine $v(t)$ for the circuit shown in below. Assume $v(0) = -1\text{mV}$.

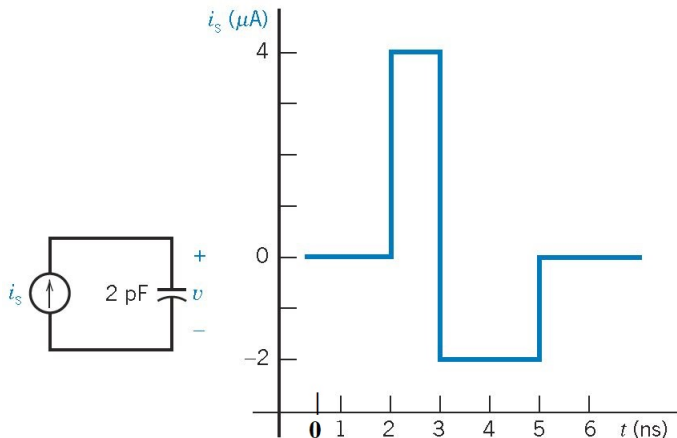


Figure: Problem 7.23 on page 295 of book

Problem 7.2-3 on page 295 - Solution

First, we would write equations of current from this graph (Note: the units of time are nano seconds and units of current are micro Amperes)

$$i_s(t) = \begin{cases} 0 & 0 < t \leq 2 \\ 4 & 2 < t \leq 3 \\ -2 & 3 < t \leq 5 \\ 0 & t > 5 \end{cases}$$

Problem 7.2-3 on page 295 - Solution

First, we would write equations of current from this graph (Note: the units of time are nano seconds and units of current are micro Amperes)

$$i_s(t) = \begin{cases} 0 & 0 < t \leq 2 \\ 4 & 2 < t \leq 3 \\ -2 & 3 < t \leq 5 \\ 0 & t > 5 \end{cases}$$

The formula for voltage across capacitor is as follows:

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

Problem 7.2-3 on page 295 - Solution

For $0 < t \leq 2$ nano seconds, we obtain the following:

$$v(t) = \frac{1}{2 \times 10^{-12}} \int_0^t 0 d\tau + (-1mV) = -10^{-3}V$$

Problem 7.2-3 on page 295 - Solution

For $0 < t \leq 2$ nano seconds, we obtain the following:

$$v(t) = \frac{1}{2 \times 10^{-12}} \int_0^t 0 d\tau + (-1mV) = -10^{-3}V$$

For $2 < t \leq 3$ nano seconds, we obtain the following:

$$v(t) = \frac{1}{2 \times 10^{-12}} \int_{2 \times 10^{-9}}^t 4 \times 10^{-6} d\tau + (-10^{-3}) = -5 \times 10^{-3} + (2 \times 10^6)t$$

Let us find the voltage at $t = 3$ nano seconds from the above equation:

$$v(3 \times 10^{-9}) = -5 \times 10^{-3} + (2 \times 10^6)(3 \times 10^{-9}) = 10^{-3}$$

Problem 7.2-3 on page 295 - Solution

For $3 < t \leq 5$ nano seconds, we obtain the following:

$$v(t) = \frac{1}{2 \times 10^{-12}} \int_{3 \times 10^{-9}}^t -2 \times 10^{-6} d\tau + (10^{-3}) = 4 \times 10^{-3} + (-10^6)t$$

Let us find the voltage at $t = 5$ nano seconds from the above equation:

$$v(5 \times 10^{-9}) = 4 \times 10^{-3} + (-10^6)(5 \times 10^{-9}) = -10^{-3}$$

For $t > 5$ nano seconds, we obtain the following:

$$v(t) = \frac{1}{2 \times 10^{-12}} \int_{5 \times 10^{-9}}^t 0 d\tau + (-10^{-3}) = -10^{-3}t$$

Problem 7.2-3 on page 295 - Solution

Finally, we summarize the result here as follows:

$$v(t) = \begin{cases} -10^{-3} & 0 < t \leq 2 \\ -5 \times 10^{-3} + (2 \times 10^6)t & 2 < t \leq 3 \\ 4 \times 10^{-3} - (10^6)t & 3 < t \leq 5 \\ -10^{-3} & t > 5 \end{cases}$$

Problem 7.2-3 on page 295 - Plot

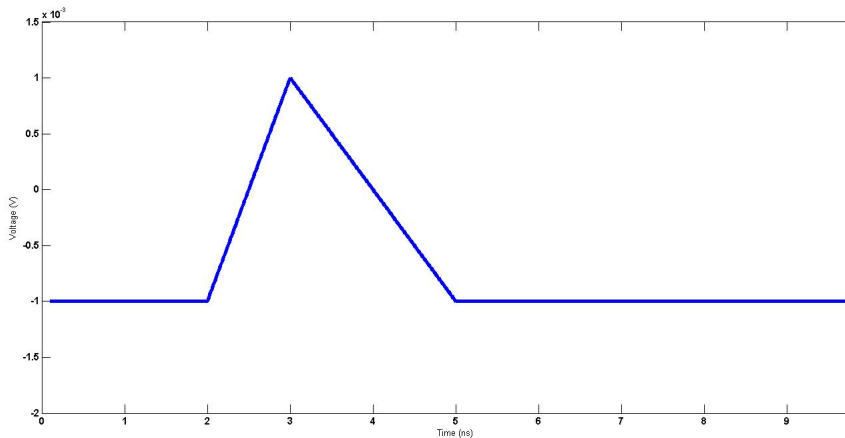


Figure: Plot of voltage

Problem 7.5-2 on page 300

A current $i(t) = 4te^{-t}\text{A}$ flows through series combination of 20Ω resistor and 0.2H inductor. Find the voltage across the combination (resistor plus inductor).

Problem 7.5-2 on page 300 - Solution

The formula is as follows:

$$\begin{aligned}v &= L \frac{di}{dt} + iR \\&= 0.2 \times \frac{d}{dt}(4te^{-t}) + (4te^{-t}) \times 20 \\&= 0.2 \times (4e^{-t} - 4te^{-t}) + 80te^{-t} \\&= 0.8e^{-t} - 0.8te^{-t} + 80te^{-t} \\&= 0.8e^{-t} + 79.2te^{-t}V\end{aligned}$$