

Quiz No: 4

Name

AS HFAEL AHMAD

Reg No:


19fw cse 1795

Section

B

— xx — xx — xx —

Ans

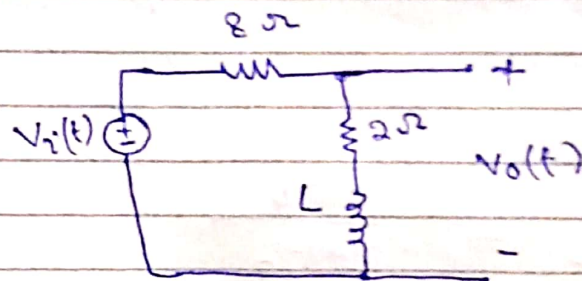

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = 0.2 \quad \frac{1+j\omega/2}{1+j\omega/p}$$

$$Z = \frac{1+j}{2} = \frac{8}{2}$$

$$\boxed{Z = 4\Omega}$$

$$P = \frac{9+5}{2} = \frac{14}{2}$$

$$P = 7$$

$$L = ?$$

V_o is the voltage drop across
series of resistor & inductor

$$V_o = \frac{2\Omega + j\omega L}{2\Omega + 8\Omega + j\omega L} V_i(t)$$

$$\frac{V_o}{V_i} = \frac{2 + j\omega L}{10 + j\omega L}$$

$$\frac{V_o}{V_i} = \frac{2}{10} \left(\frac{1 + j\omega L/2}{1 + j\omega L/10} \right)$$

$$H(\omega) = \frac{V_o}{V_i} = 0.2 \left(\frac{1 + j\omega L/2}{1 + j\omega L/10} \right) \quad \text{--- eq (1)}$$

This is the network function, Now the given function is,

$$H(\omega) = 0.2 \left(\frac{1 + j\omega/2}{1 + j\omega/7} \right) \quad \text{put values}$$

$$H(\omega) = 0.2 \left(\frac{1 + j\omega/4}{1 + j\omega/7} \right) \quad \text{--- eq (2)}$$

Compare eq (1) & (2)

$$\cancel{0.2} \left(\frac{1 + j\omega L/2}{1 + j\omega L/10} \right) = \cancel{0.2} \left(\frac{1 + j\omega/4}{1 + j\omega/7} \right)$$

Compare numerator.

$$\cancel{1 + j\omega L/2} = \cancel{1 + j\omega/4}$$

$$L/2 = \frac{1}{4}$$

$$L = \frac{2}{4}$$

$$\boxed{L = 0.5}$$

Now compare denominator.

$$\cancel{1 + j\omega L/10} = \cancel{1 + j\omega/7}$$

$$\frac{L}{10} = \frac{1}{7}$$

$$L = \frac{10}{7}$$

$$\boxed{L = 1.428}$$

As these equations gives d/p values
So this equation cannot be solved
for my Reg No

———— xx ———— xx ———— v
the ENID
 > >

By ASHFAQ AHMAD
Reg No: 19PWCSE1795
