

University of engineering & technology Peshawar



Circuit & system-1

Final-term paper

Spring 2020

Submitted by: Ashfaq Ahmad

Section: B

Reg No: 19PWCSE1795

Semester: 2nd

“On my honor, as a student of University of Engineering and Technology Peshawar, I have neither given nor received unauthorized assistance on this academic work”

Student signature: _____

**Submitted to:
prof: salman ahmad**

Department Of Computer System Engineering

Name: ASHFAAQ AHMAD
Reg No: 19PWCE1795

(Page No 1)

Answer No 1:

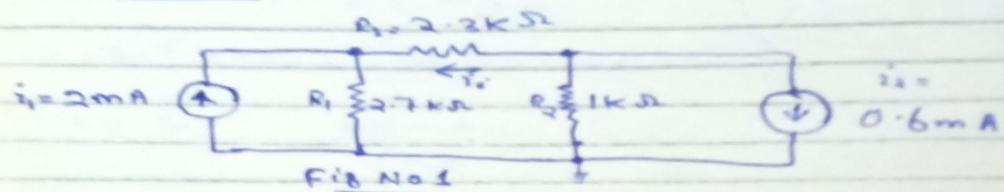



Fig No 1

Now According to Source - Transformation
 $V_{S1} = i_1 R_1$ put values

$$V_{S1} = 2 \times 10^{-3} \times 2.7 \times 10^3$$

$$V_{S1} = 5.4\text{V}$$

So figure NO 1 become

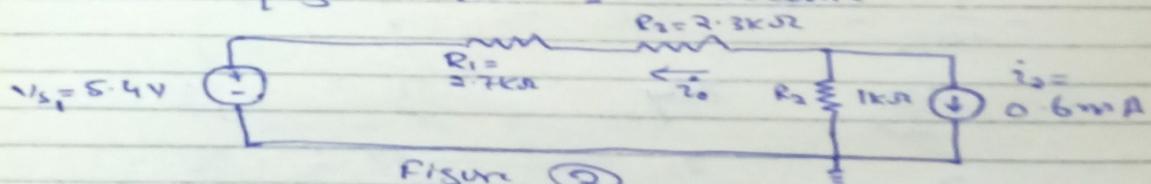

Now we can further Simplify Figure ②
by Using Source transformation

$$V_{S2} = i_2 \times R_2 \quad \text{put value}$$

$$V_{S2} = 1 \times 10^{-3} \times 0.6 \times 10^3$$

$$V_{S2} = 0.6\text{V}$$

$$V_{S2} = 0.6\text{V}$$

Name : ASHFAAQ Ahmad
 Reg NO: 19PWCSE1795

Page ②

Now figure ② become.

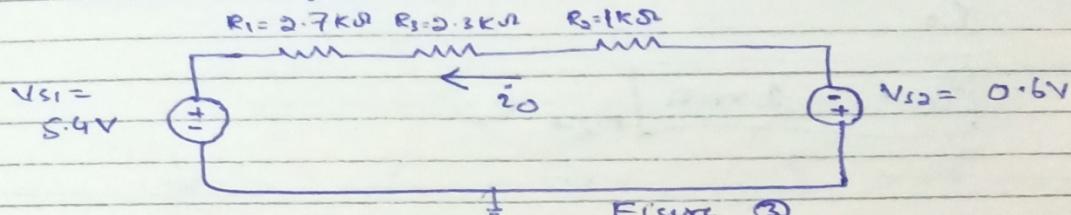



Figure ③

Now equivalent resistance of R_1, R_2, R_3 is

$$R_E = (2.7\text{k} + 2.3\text{k} + 1\text{k})\text{\Omega}$$

$$R_E = 6\text{k}\Omega$$

Figure ③ becomes,

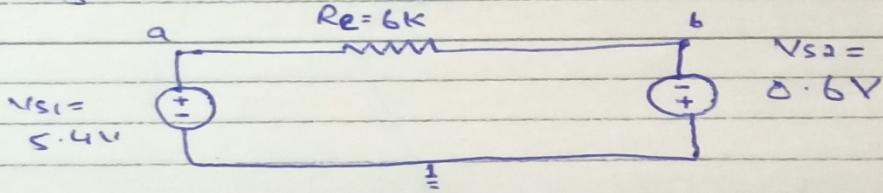

Now i_o is given by

$$i_o = \frac{V_{S1} - V_{S2}}{R_E}$$

$$V_{S1} = 5.4\text{V}$$

$$V_{S2} = -0.6\text{V} \quad (\text{opposite in direction})$$

$$\text{So } i_o = \frac{5.4 - (-0.6)}{6 \times 10^3} = \frac{6.0}{6 \times 10^3 \text{ }\Omega}$$

$$i_o = 1\text{mA}$$

$$P + T + O$$

Name: ASHFAQ AHMAD
Reg. NO: 19PW CSE 1795.

Page 3

Since it is opposite in direction
So

$$I_o = -1 \text{ mA}$$


Ans

— XXX — XXX — XXX —

Name ASHFAQS AHMAD
Reg NO: 19PW CSE 1795

Page 4

Answer No 2:

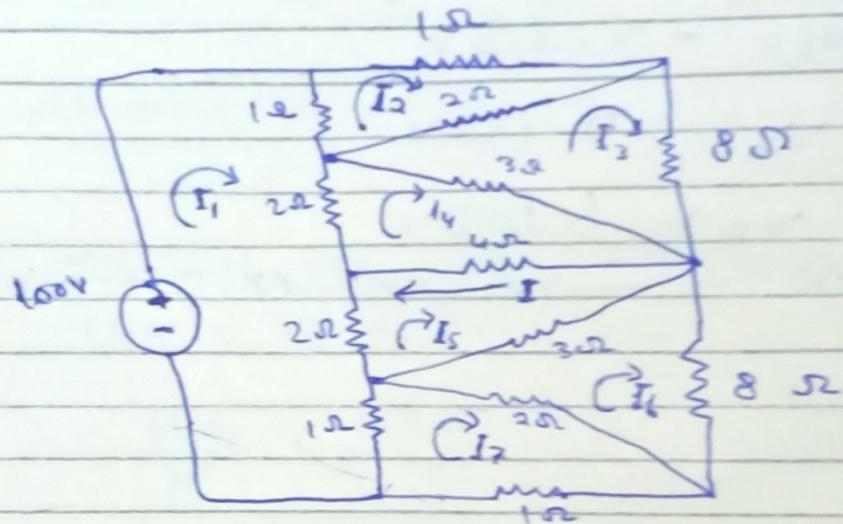

All mesh current are labeled
and we are going clockwise
in each mesh

Mesh 1: (containing voltage source)

$$-100V + 1(I_1 - I_2) + 2(I_1 - I_4) + 2(I_1 - I_5) + 1(I_1 - I_7) = 0$$

$$I_1 + I_2 + 2I_1 - 2I_4 + 2I_1 - 2I_5 + I_1 - I_4 = 100$$

$$6I_1 - I_2 - 2I_4 - 2I_5 - I_7 = 100 \quad \text{①}$$

Name Asif Rafeq Ahmad
Reg No. 19PW CSE 1798

Page 5

Mesh 2:

$$1(I_2 - I_1) + I_2 + 2(I_2 - I_3) = 0$$

$$I_2 - I_1 + I_2 + 2I_2 - 2I_3 = 0$$

$$-I_1 + 4I_2 - 2I_3 = 0 \rightarrow \text{eq } ②$$

Mesh 3:

$$3(I_3 - I_4) + 2(I_3 - I_2) + 8I_3 = 0$$

$$3I_3 - 3I_4 + 2I_3 - 2I_2 + 8I_3 = 0$$

$$-2I_2 + 13I_3 - 3I_4 = 0 \rightarrow \text{eq } ③$$

Mesh 4:

$$2(I_4 - I_1) + 3(I_4 - I_3) + 4(I_4 - I_5) = 0$$

$$2I_4 - 2I_1 + 3I_4 - 3I_3 + 4I_4 - 4I_5 = 0$$

$$-2I_1 - 3I_3 + 9I_4 - 4I_5 = 0 \rightarrow$$

eq ④

Mesh 5:

$$2(I_5 - I_1) + 4(I_5 - I_4) + 3(I_5 - I_6) = 0$$

Name Asif RAo Ahmed
Reg No: 19PW CSE 1795 page ⑥

$$2I_5 - 2I_1 + 4I_5 - 4I_4 + 3I_5 - 3I_1 = 0$$

$$-2I_1 - 4I_4 + 9I_5 - 3I_6 = 0 \rightarrow \text{eq } ⑤$$

Mesh 6:

$$2(I_6 - I_7) + 4_3(I_6 - I_5) + 8I_6 = 0$$

$$2I_6 - 2I_7 + 3I_6 - 3I_5 + 8I_6 = 0$$

$$-3I_5 + 13I_6 - 2I_7 = 0 \rightarrow \text{eq } ⑥$$

Mesh 7:

$$I_7 + 2(I_7 - I_1) + 2(I_7 - I_6) = 0$$

$$I_7 + 2I_7 - 2I_1 + 2I_7 - 2I_6 = 0$$

$$-5I_1 - 2I_6 + 4I_7 = 0 \rightarrow \text{eq } ⑦$$

Now we have ⑦ eq

$$P + T_F = 0$$

Name ACHALAKA Akumard

Reg No: 13PWCSE 1798

Page 3

$$6I_1 - I_2 + 0I_3 - 2I_4 - 2I_5 \\ + 0I_6 - 1I_7 = 100$$

$$-1I_1 + 4I_2 - 2I_3 + 0I_4 + 0I_5 \\ - 0I_6 + 0I_7 = 0$$

$$0I_1 - 2I_2 + 13I_3 - 3I_4 + 0I_5 \\ - 0I_6 + 0I_7 = 0$$

$$-2I_1 + 0I_2 + 6I_3 - 4I_4 - 3I_6 = 0$$

$$-3I_5 + 13I_6 - 2I_7 = 0 \\ -1I_1 - 2I_6 + 4I_7 = 0$$

I have used MATLAB To
solve above equation, the
code is pasted in next
page

$$I_4 = -3.092784$$

$$I_5 = -3.092784$$

Current through 4Ω Resister is,

$$I = I_4 - I_5$$

$$P + T + D$$

Name ASHTFAR Ahmad

Reg NO: 19DW CSE 1798

Page 2

$$I = -3.092784 + 0.39784$$

$$\boxed{I = 0 A}$$

Ans

— xx — xx — xx — xy

the END


7 }

```
clc;
clear all;
abc = [6 -1 0 -2 -2 0 -1;
        -1 4 -2 0 0 0 0;
        0 -2 13 -3 0 0 0;
        -2 0 -3 9 -4 0 0;
        -2 0 0 -4 9 -3 0;
        0 0 0 0 -3 13 -2;
        -1 0 0 0 0 -2 4];
n = [100 0 0 0 0 0 0]';
I = inv(abc) * n;
fprintf('Current I4 = %f\n', I(4));
fprintf('Current I5 = %f\n', I(5));
fprintf('Current through 4 ohm resistor
is %f\n', I(4) - I(5));
```

Name ASHFAQ AHMAD
Reg No: 19PUCE1795

Page 9

Answer No 3:

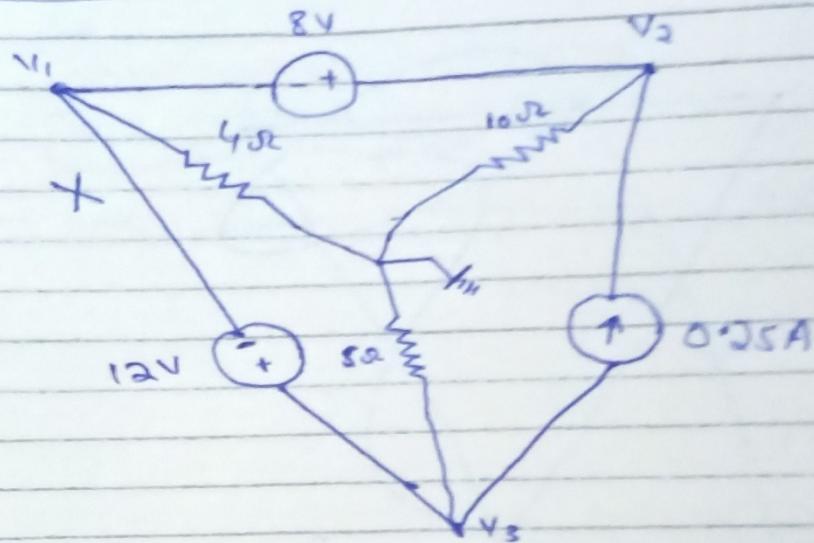

Applying KCL to the Supernode gives -

$$\frac{V_2}{10} + \frac{V_1}{4} + \frac{V_3}{5} = 0 \quad \text{--- (1)}$$

By inspection, it is clear that

$$\begin{aligned} V_2 - V_1 &= 8V \\ \Rightarrow V_2 &= V_1 + 8 \quad \text{--- (2)} \\ V_3 - V_1 &= 12V \end{aligned}$$

$$\Rightarrow V_3 = V_1 + 12 \quad \text{--- (3)}$$

Substituting in Eq (2) & Eq (3)

P-TFO

Name: ASHFAQ AHMAD
Reg No: 19PW CSE 1795

Page 10

$$\frac{V_1 + 8}{10} + \frac{V_1}{4} + \frac{V_1 + 12}{5} = 0$$

$$\frac{2(V_1 + 8) + 5V_1 + 4(V_1 + 12)}{20} = 0$$

$$2V_1 + 16 + 5V_1 + 4V_1 + 48 = 0$$
$$11V_1 + 64 = 0$$

$$\frac{11V_1}{11} = -\frac{64}{11}$$

$$V_1 = -5.818V$$

Put V_1 in eq ②

$$V_2 = V_1 + 8$$

$$V_2 = -5.818 + 8$$

$$V_2 = 2.182V$$

Now put V_1 in eq ③
 $V_3 = V_1 + 12$

$$V_3 = -5.818 + 12$$

$$V_3 = 6.182V$$

OR

$$P - IT + 0$$

Name: ASHFAQ Ahmad
Reg No: 19PWCSE1795

Page (11)

Thus Node Voltages are

$$V_1 = -5.818 \text{ V}$$

$$V_2 = 2.182 \text{ V}$$

$$V_3 = 6.182 \text{ V}$$

—xx— —xx— —xx— —xx—