

Name :

Reg NO :

Section :

Paper :

ASHFAQ AHMA
19PWCE 1795
B

CS-II

(2)
Ans

Given:

$$R = 10 \Omega$$


$$L = 1 \text{ mH}$$

$$C = \frac{1+7+9+5}{4} \times 10 \text{ mF}$$

$$C = 55 \text{ mF}$$

$$V_s = 10 \angle 0^\circ$$

$$\omega = 1000 \text{ rad/s}$$

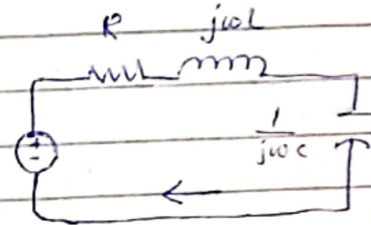

Sol

first we find Z_L & Z_C .

$$Z_L = j\omega L \quad \text{put values}$$

$$Z_L = j(1000)(1 \times 10^{-3}) \Omega$$

$$Z_L = 1j \Omega$$

Now

$$Z_C = \frac{1}{j\omega C} \quad \text{put values}$$

$$= \frac{1}{j(1000)(55 \times 10^{-3})}$$

$$= -j \frac{1}{55} \Omega$$

$$Z_C = -j 0.01818 \Omega$$

Now we find equivalent impedance
P + T P O

$$Z_e = R + Z_c + Z_L$$

$$Z_e = 10 + 1j + (-j0.01818)$$

$$Z_e = 10 + 1j - j0.01818$$

$$Z_e = 10 + j0.982 \Omega$$

Now current is given by

$$I(\omega) = \frac{V_s(\omega)}{Z_e(\omega)} \quad \text{put values}$$


$$I(\omega) = \frac{10 \angle 0^\circ}{(10 + j0.982) \Omega}$$

$$I(\omega) = \frac{10 \angle 0^\circ}{10.048 \angle 5.6^\circ}$$

$$I(\omega) = 0.995 \angle -5.6^\circ$$

$$I(t) = 0.995 \cos(1000t - 5.6^\circ) \text{ A} \quad \text{Ans}$$

Phasor plot

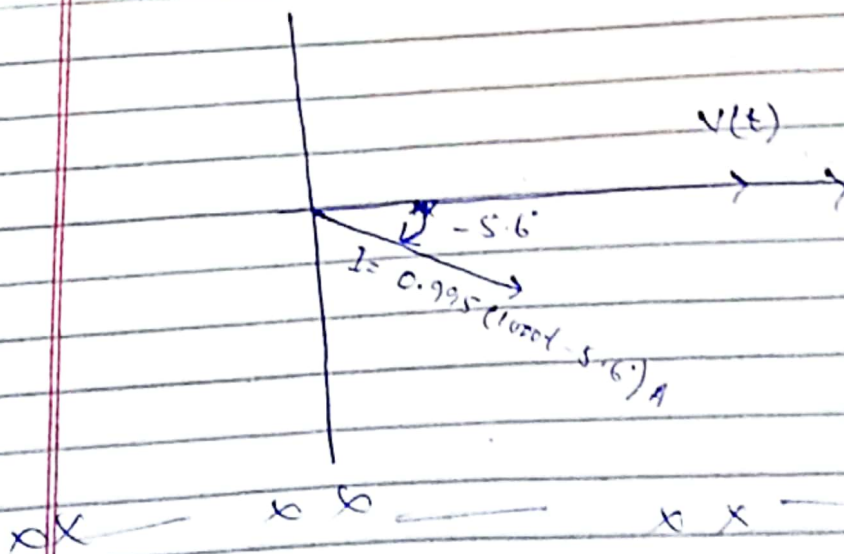

Q₄

Given


$$I = ?$$

$$V_s = 50 \angle 120^\circ \text{ V rms}$$

$$\text{Complex power} = S = ??$$

$$X_c = \left(\frac{1+7+9+5}{4} \right) \Omega$$

$$X_c = 5.5 \Omega$$

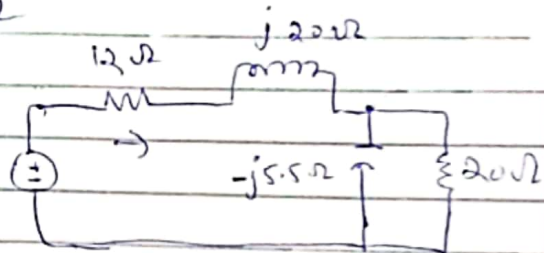

Sol

Consider source voltage

$$V = 50 \angle 120^\circ \text{ V rms}$$

Calculate maximum Amplitude of

$$V_m = \sqrt{2} V \text{ rms}$$

$$V_m = 50 \sqrt{2} \text{ V rms}$$

Calculate equivalent Z_{eq}

$$Z_{eq} = (12 + j20) + \frac{(20)(-j5.5)}{20 - j5.5}$$

$$Z_{eq} = (12 + j20) + \frac{110 \angle -90^\circ}{22.36 \angle -26.56^\circ}$$

$$Z_{eq} = (12 + j20) + (4 - j8)$$

$$Z_{eq} = 16 + j12$$

Now calculate $I_{max} = ???$

$$P \quad + \quad T \quad + \quad 0$$

$$I_m = \frac{V_m}{Z_{eq}} \quad \text{put values}$$



$$I_m = \frac{50\sqrt{2} \angle 120^\circ}{16 + j12}$$

After solving we get

$$I_m = 3.535 \angle 83.13^\circ \text{ A}$$

Now Calculate RMS value of the current.

$$I_m = \frac{I_m}{\sqrt{2}} = \frac{3.535 \angle 83.13^\circ}{\sqrt{2}}$$

$$I_m = 2.5 \angle 83.13^\circ \text{ A}$$

* Therefore, rms value of current is $2.5 \angle 83.13^\circ \text{ A}$.

* And Maximum value of current is $3.535 \angle 83.13^\circ \text{ A}$.

Now we find Complex power delivered by source
As

$$S = V I^*$$

$$S = \frac{V_m I_m}{2} \angle \theta_v - \theta_i$$

Now put values of V_m , I_m we get

page (5)

$$S = \frac{(50\sqrt{2})(3535)}{2} \angle (120^\circ - 83.13^\circ)$$

$$= 125 \angle 36.87^\circ \text{ VA}$$

$$= 125 \cos 36.87^\circ + j 125 \sin 36.87^\circ$$

$$S = 100 + j 75 \text{ VA}$$

So

$$S = 100 + j 75 \text{ VA}$$

Ans

xx

xx

xx

xx


3
Ans

Given:

$$V_o(t) = ?$$

$$\omega = (1+7+9+5) \times 10^3 \text{ rad/s}$$

$$\omega = 220 \text{ rad/s}$$

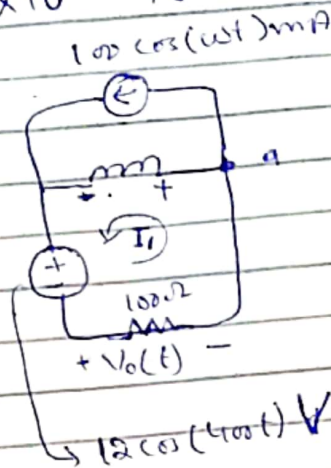

Sol

first we find X_L

$$X_L = j\omega L$$

$$X_L = j(220)(0.375) \Omega$$

$$X_L = j82.5 \Omega$$

Now Apply KVL to lower mesh

$$-I_1(82.5) - 12 \angle 0^\circ - V_o(t) = 0$$

$$V_o(t) = -I_1(j82.5) - 12 \angle 0^\circ \quad \text{--- (1)}$$

Now we find I_1
Apply KCL at node (a)


$$I_1 = \frac{12 \angle 0^\circ + 100 \angle 0^\circ}{j82.5 \Omega}$$

Given

$$V_{t} = ? \quad Z_{t} = ?$$

$$X_L = 1 + 7 + 9 + 5 = 22 \Omega$$

$$X_C = 5.5 \Omega$$

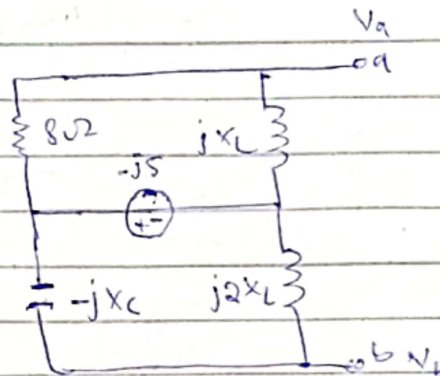

Sol

$$V_t = V_a + V_b \quad \text{--- (1)}$$

$$V_a = \frac{-j5}{8 + jX_L} \times jX_L$$

$$V_a = \frac{-j5}{8 + j22} \times j22$$

$$V_a = \frac{-j^2 110}{8 + j22}$$

$$V_a = \frac{110}{23.4}$$

$$V_a = \frac{110 \angle 0^\circ}{23.4 \angle 70^\circ}$$

$$V_a = 4.70 \angle -70^\circ$$

$$V_b = \frac{-j5}{j44 - j8.5} \times j44$$

Pa 8 (9)

$$V_b = \frac{-j5}{j39.5} \times j44$$

$$V_b = \frac{220 \angle 0^\circ}{39.5 \angle 90^\circ}$$

$$V_b = 5.56 \angle -90^\circ$$


Now

$$V_t = V_a + V_b$$

$$V_t = 4.70 \angle -70^\circ + 5.56 \angle -90^\circ$$

Now $Z_t = ??$

for Z_t circuit becomes

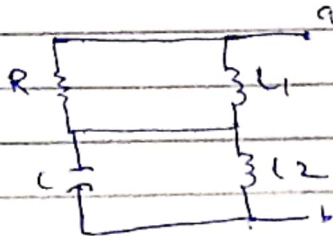


$$R \parallel L_1 = \frac{1}{\frac{1}{R} + \frac{1}{X_{L_1}}}$$

$$= \frac{R X_{L_1}}{R + X_{L_1}}$$

$$= \frac{8 + 22j}{8(22j)}$$

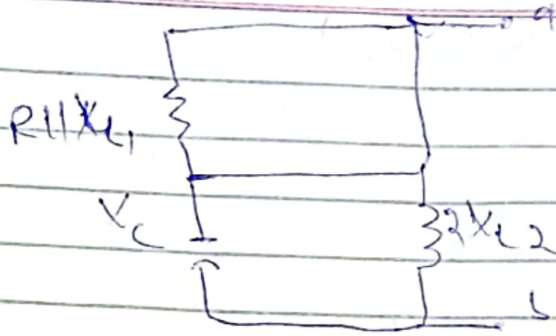
$$R \parallel L_1 = \frac{8 + 22j}{176j}$$



Now Xc in parallel with $2X2$ So

$$Xc \parallel 2X2 = \frac{Xc + 2X2}{(Xc)(2X2)}$$

$$= \frac{-j5.5 + j44}{(-j5.5)(j44)}$$

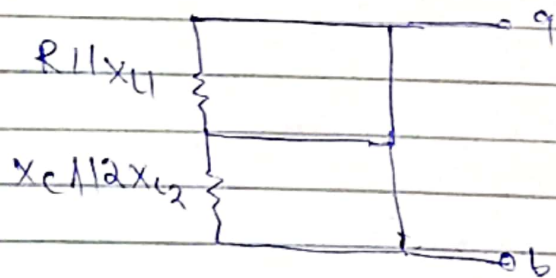

$$\frac{1}{Zc} = \frac{1}{R1 \parallel X1} + \frac{1}{Xc \parallel 2X2}$$

Any

the END