

Selecting

- Selecting of data or information is a critical function in digital systems and computers
- Circuits that perform selecting have:
 - A set of information inputs from which the selection is made
 - A single output
 - A set of control lines for making the selection
- Logic circuits that perform selecting are called *multiplexers*


Multiplexers

- A multiplexer selects information from an input line and directs the information to an output line
- A typical multiplexer has n control inputs (S_{n-1}, \dots, S_0) called *selection inputs*, 2^n information inputs (I_{2^n-1}, \dots, I_0), and one output Y
- A multiplexer can be designed to have m information inputs with $m < 2^n$ as well as n selection inputs

Multiplexer (cont.)



- “Selects” binary information from one of many input lines and directs it to a single output line.
- Also known as the “selector” circuit,
- Selection is controlled by a particular set of input lines whose # depends on the # of the data input lines.
- For a 2^n -to-1 multiplexer, there are 2^n data input lines and n selection lines whose bit combination determines which input is selected.

Multiplexer (cont.)

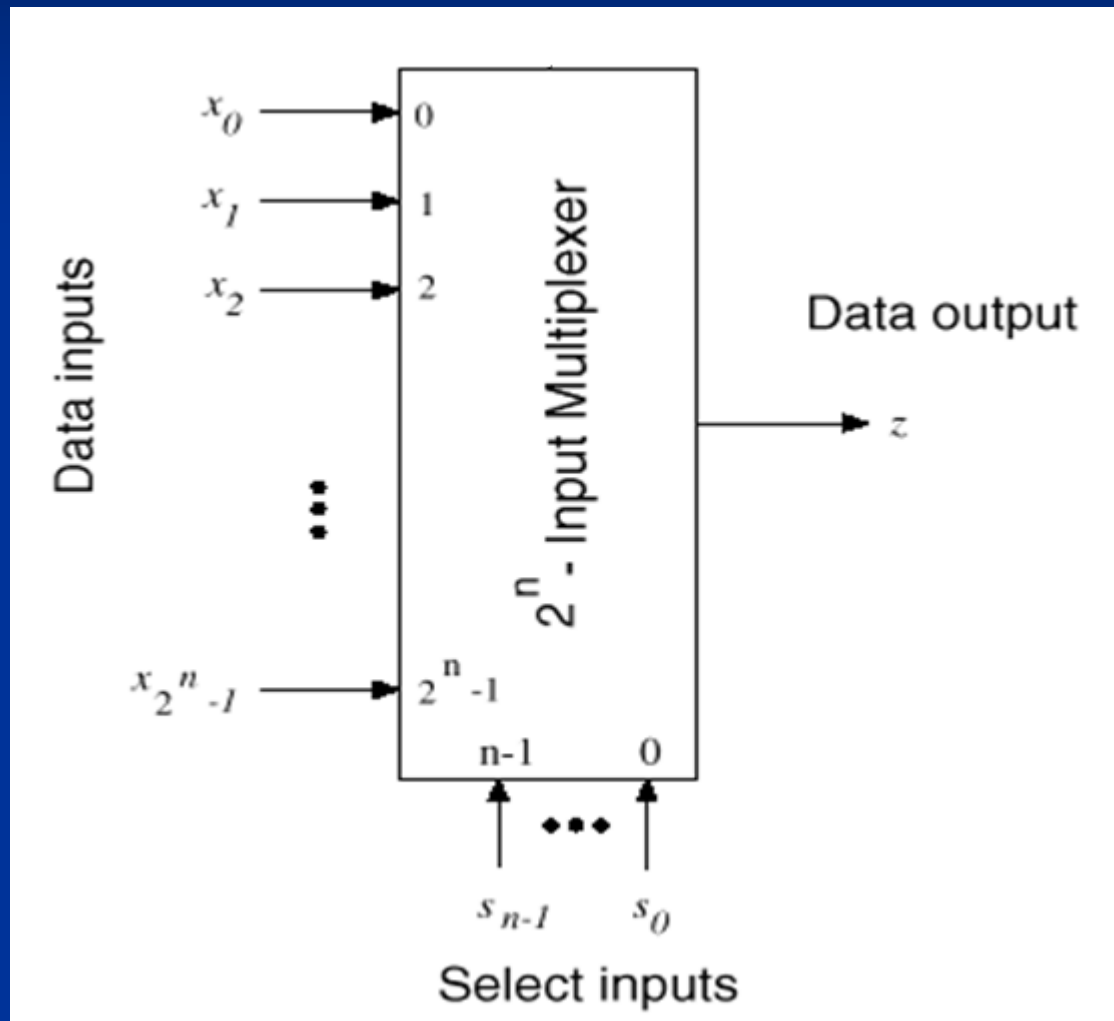


2-to-1 MUX Design

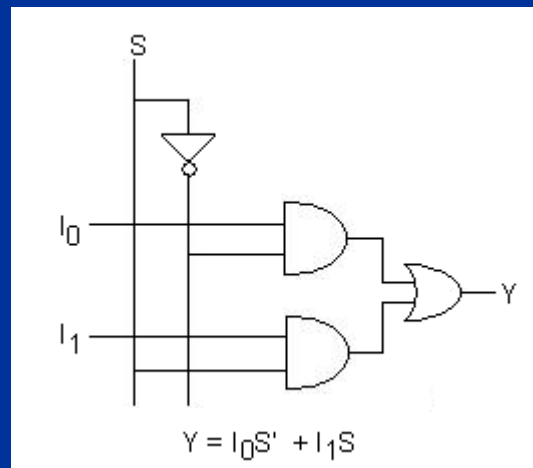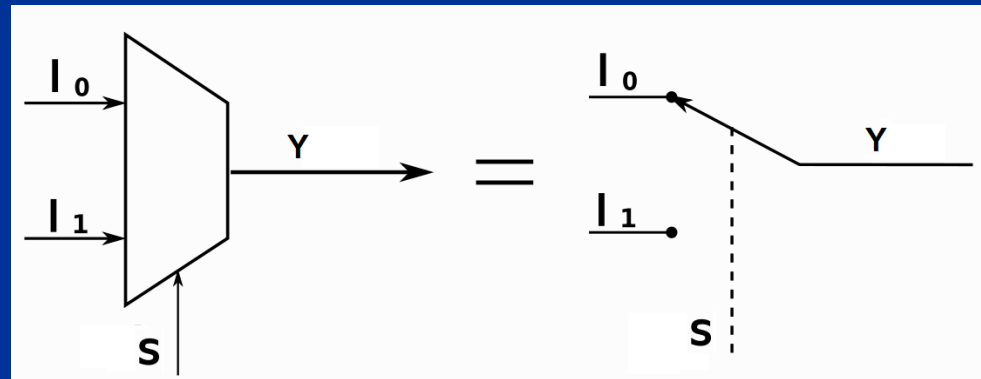- Since $2 = 2^1$, $n = 1$
- The single selection variable S has two values:
 - $S = 0$ selects input I_0
 - $S = 1$ selects input I_1
- The equation:
$$Y = S'I_0 + SI_1$$
- The circuit:




S	Y
0	I0
1	I1


4-to-1 MUX Design

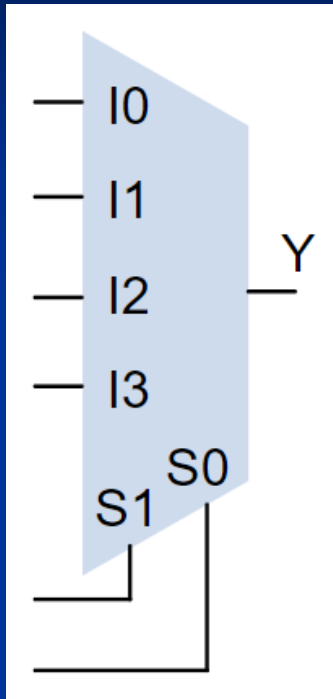


S1	S0	Y
0	0	I0
0	1	I1
1	0	I2
1	1	I3

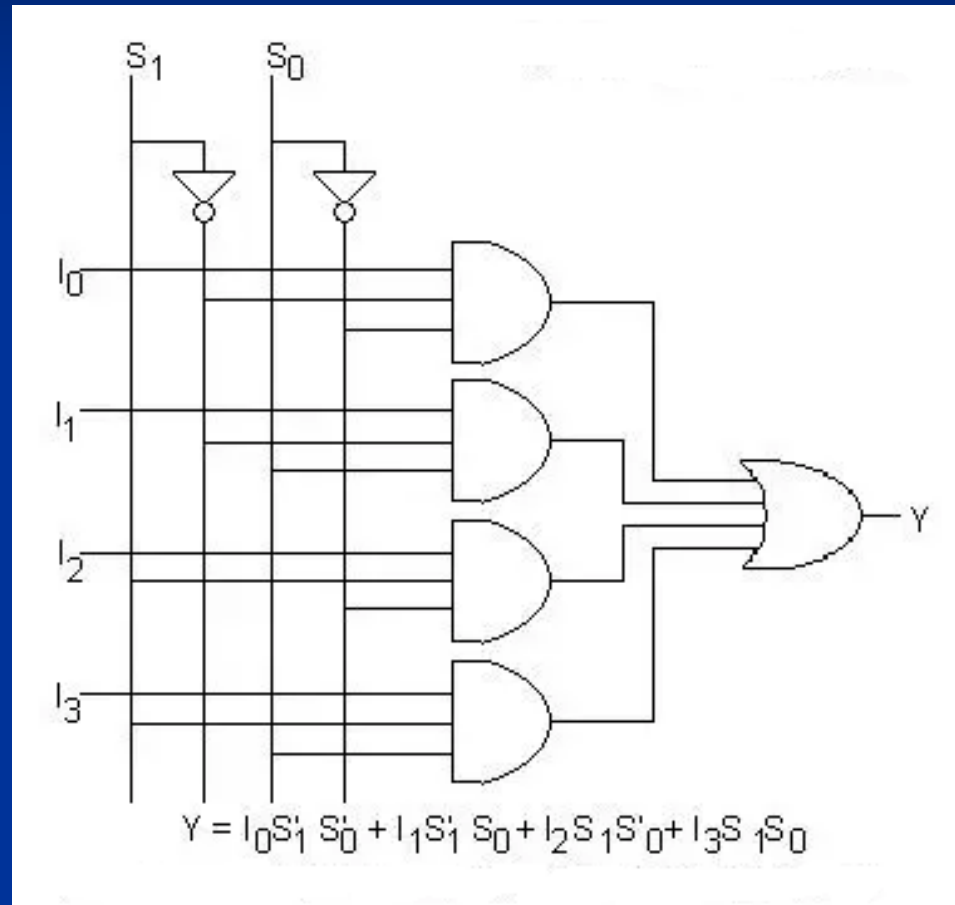

8-to-1 MUX Design

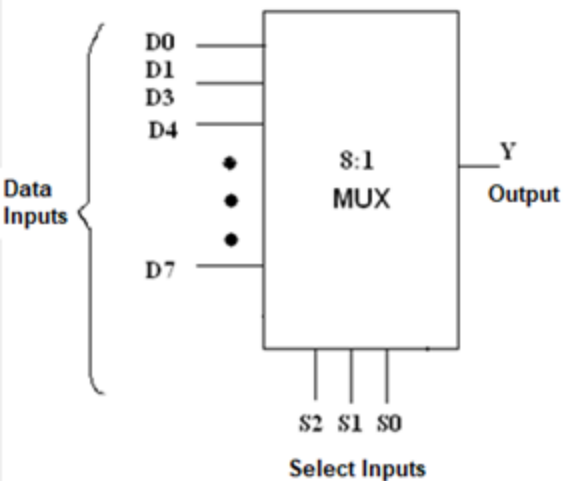

Select Inputs			Output
S2	S1	S0	Y
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

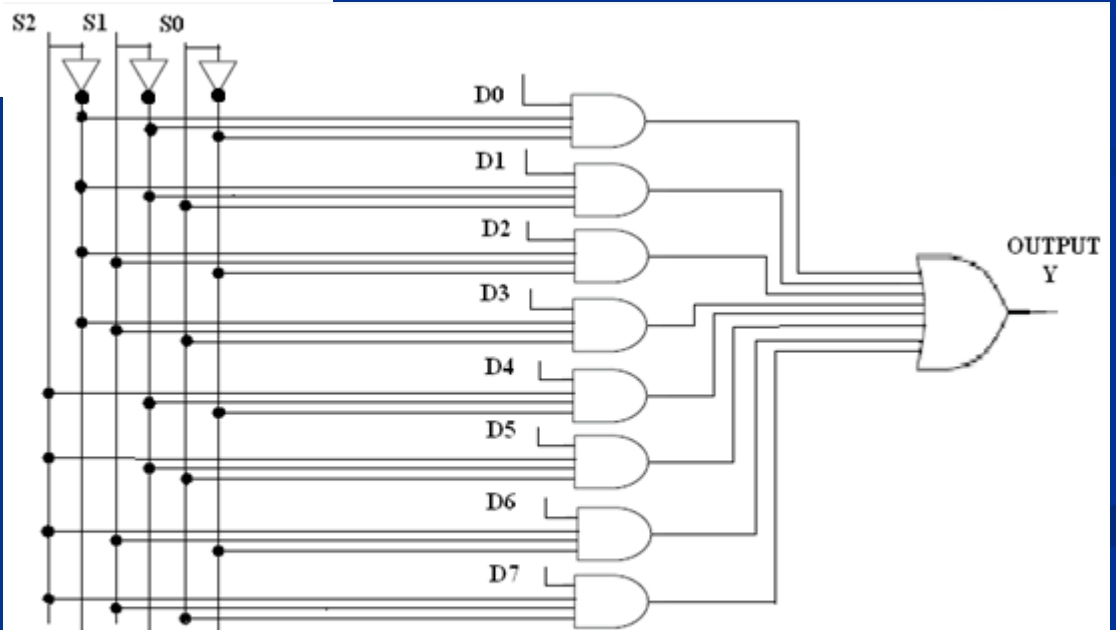


$$Y = \overline{S_2} \overline{S_1} \overline{S_0} D_0 + \overline{S_2} \overline{S_1} S_0 D_1 + \overline{S_2} S_1 \overline{S_0} D_2 + \overline{S_2} S_1 S_0 D_3 + S_2 \overline{S_1} \overline{S_0} D_4 + S_2 \overline{S_1} S_0 D_5 + S_2 S_1 \overline{S_0} D_6 + S_2 S_1 S_0 D_7$$

De-Multiplexers

- De-Multiplexer is a combinational circuit that performs the reverse operation of Multiplexer.
- It has single input, 'n' selection lines and maximum of 2^n outputs. The input will be connected to one of these outputs based on the values of selection lines.
- Since there are 'n' selection lines, there will be 2^n possible combinations of zeros and ones. So, each combination can select only one output.

1-to-4 De-MUX Design

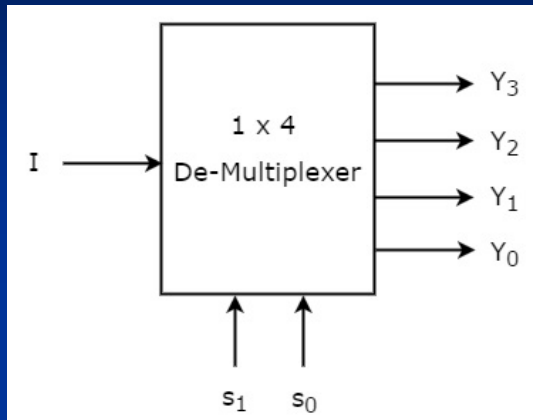

Selection Inputs		Outputs			
s ₁	s ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

$$Y_3 = s_1 s_0 I$$

$$Y_2 = s_1 s_0' I$$

$$Y_1 = s_1' s_0 I$$

$$Y_0 = s_1' s_0' I$$

