



**University of engineering & technology Peshawar**

**Digital Logic & computer Design-theory**

**Assignment no#02**

**Spring 2020**

**Submitted by: Ashfaq Ahmad**

**Section: B**

**Reg No: 19PWCSE1795**

**Semester: 3<sup>rd</sup>**

**“On my honor, as a student of University of Engineering and Technology Peshawar, I have neither given nor received unauthorized assistance on this academic work”**

Student signature: \_\_\_\_\_

**Submitted to:  
Eng: rehmat sab**

**Department Of Computer System Engineering**



Ans:

Truth table						
x	y	z	F <sub>1</sub>	Symbol	minterm	
0	0	0	0	m <sub>0</sub>	$\bar{x}\bar{y}\bar{z}$	
0	0	1	0	m <sub>1</sub>	$\bar{x}\bar{y}z$	
0	1	0	1	m <sub>2</sub>	$\bar{x}y\bar{z}$	
0	1	1	1	m <sub>3</sub>	$\bar{x}yz$	
1	0	0	1	m <sub>4</sub>	$x\bar{y}\bar{z}$	
1	0	1	0	m <sub>5</sub>	$x\bar{y}z$	
1	1	0	1	m <sub>6</sub>	$xy\bar{z}$	
1	1	1	0	m <sub>7</sub>	$xyz$	

Table 1.1

For F<sub>1</sub>:

$$\begin{aligned}
 F_1(x, y, z) &= \sum m(m_2, m_3, m_4, m_6) \\
 &= \sum m(2, 3, 4, 6) \\
 &= (\bar{x}y\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xy\bar{z})
 \end{aligned}$$

$$F_1(x, y, z) = \bar{x}'y(z' + z) + xz'(y' + y)$$

According to boolean law

$$z' + z = 1 \quad \& \quad y' + y = 1 \quad \text{So}$$

$$F_1(x, y, z) = \bar{x}'y + xz'$$

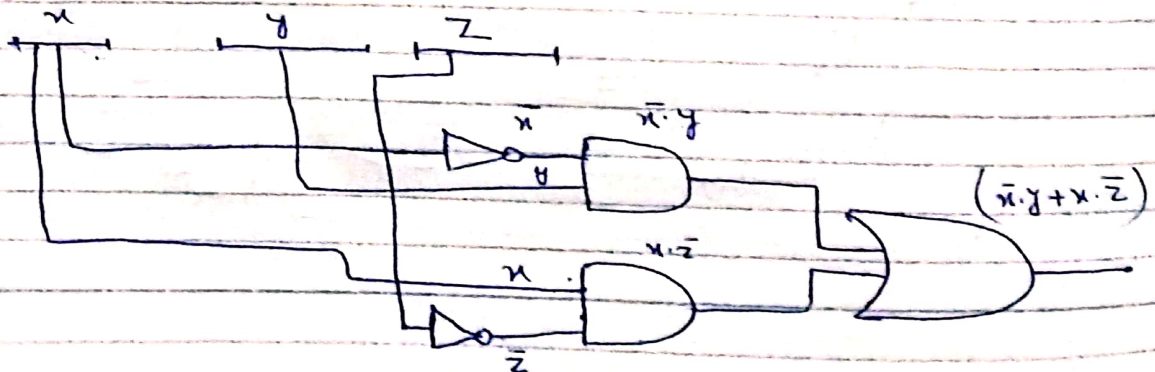


Table for more functions.

x	y	z	F <sub>2</sub>	F <sub>3</sub>	F <sub>4</sub>	F <sub>5</sub>	F <sub>6</sub>	F <sub>7</sub>	F <sub>8</sub>	F <sub>9</sub>	F <sub>10</sub>
0	0	0	0	1	0	1	0	0	0	0	0
0	0	1	1	1	0	1	0	1	0	1	0
0	1	0	0	0	1	0	1	1	0	0	0
0	1	1	1	0	0	0	1	0	1	1	0
1	0	0	1	0	1	0	0	1	0	0	1
1	0	1	0	1	0	0	0	0	1	1	1
1	1	0	0	1	1	0	0	1	1	0	0
1	1	1	1	0	0	1	1	0	0	1	1


Table 1.2

For F<sub>3</sub>:

the minterm for F<sub>3</sub> from table 1.2

$$\begin{aligned}
 F_3(x, y, z) &= \sum m(0, 1, 5, 6) \\
 &= (\bar{x}\bar{y}\bar{z} + \bar{x}\bar{y}z + x\bar{y}z + x\bar{y}\bar{z}) \\
 &= \bar{x}\bar{y}(\bar{z} + z) + x\bar{y}z + x\bar{y}\bar{z}
 \end{aligned}$$
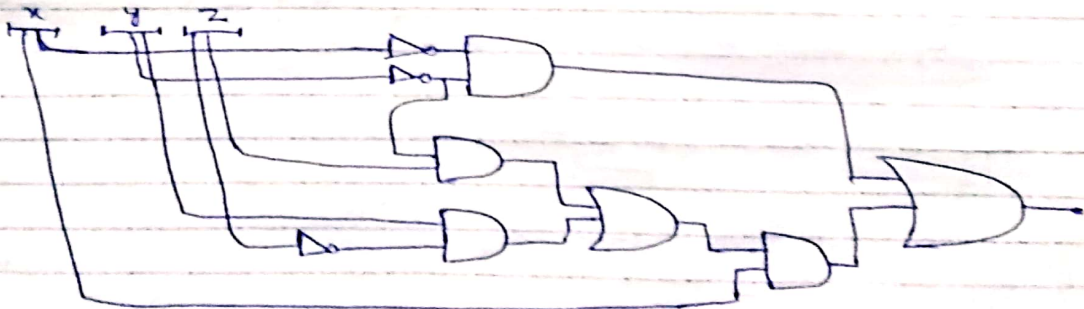
$$\boxed{F_3(x, y, z) = \bar{x}\bar{y}(1) + x(\bar{y}z + \bar{y}\bar{z})}$$



page (4)

For  $F_2$ :

the minterm for  $F_2$  from table  
 $F_2(x, y, z) = \sum m(1, 3, 4, 7)$


$$= (\bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}\bar{z} + xyz)$$

$$= \bar{x}\bar{y}\bar{z} + \bar{x}yz + xyz + x\bar{y}\bar{z}$$

$$= \bar{x}\bar{y}\bar{z} + yz(\bar{x} + x) + x\bar{y}\bar{z}$$

$$= \bar{x}\bar{y}\bar{z} + yz + x\bar{y}\bar{z}$$
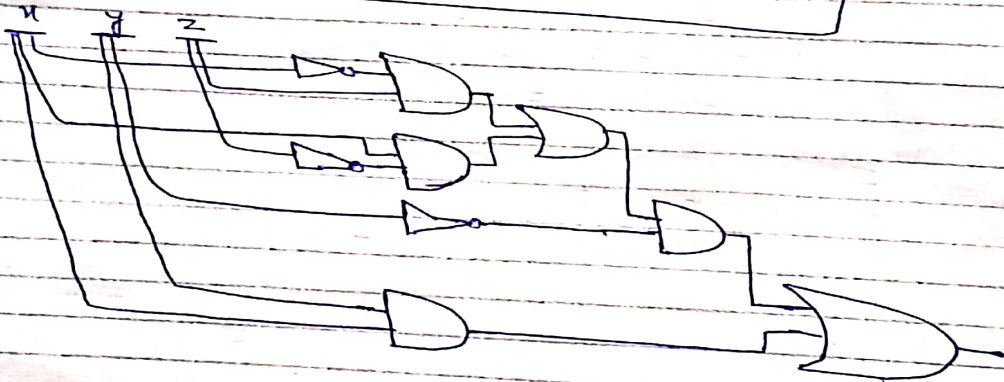
$$F_2(x, y, z) = \bar{y}(\bar{x}z + x\bar{z}) + yz$$





F<sub>4</sub>:

$$F_4(x, y, z) = \sum m(2, 4, 6)$$

$$= (\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z)$$
~~$$= (\bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z)$$~~


$$F_4(x, y, z) = \bar{z}(\bar{x}y + x\bar{y} + x\bar{y})$$

~~Circuit Diagram~~

$$= \bar{z}(\bar{x}y + x(\bar{y} + y))$$

$$F_4(x, y, z) = \bar{z}(\bar{x}y + x)$$

Circuit Diagrams

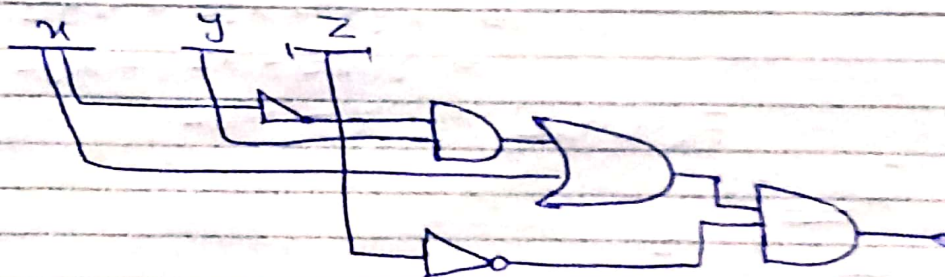

F<sub>5</sub>:

$$F_5(x, y, z) = \sum m(0, 1, 7)$$


$$= (\bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + xyz)$$

$$= (\bar{x}\bar{y}\bar{z} + z(\bar{x}\bar{y} + xy))$$

$$F_5(x, y, z) = \bar{x}\bar{y}\bar{z} + z$$

Page (6)

Circuit diagrams

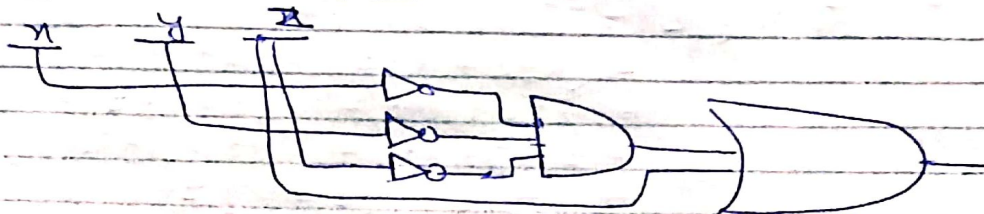

F<sub>6</sub>:

$$F_6(x, y, z) = \sum m(2, 3, 7)$$

$$= \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}z$$

$$= \bar{x}\bar{y}\bar{z} + x\bar{y}z + \bar{x}yz$$

$$= y(\bar{x}\bar{z} + xz) + \bar{x}yz$$

$$= y + \bar{x}yz$$

$$F_6(x, y, z) = y(1 + \bar{x}z)$$

As  $1 + \text{anything} = 1$  so


$$F_6(x, y, z) = y$$

(7)

F<sub>7</sub>:


$$\begin{aligned}
 F_7(x, y, z) &= \sum m(1, 2, 4, 6) \\
 &= (\bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z}) \\
 &= \bar{x}\bar{y}z + \bar{z}(\bar{x}y + x\bar{y} + xy) \\
 &= \bar{x}\bar{y}z + \bar{z}(\bar{x}y + x(\bar{y} + y)) \\
 F_7(x, y, z) &= \bar{x}\bar{y}z + \bar{z}(\bar{x}y + x)
 \end{aligned}$$

Circuit

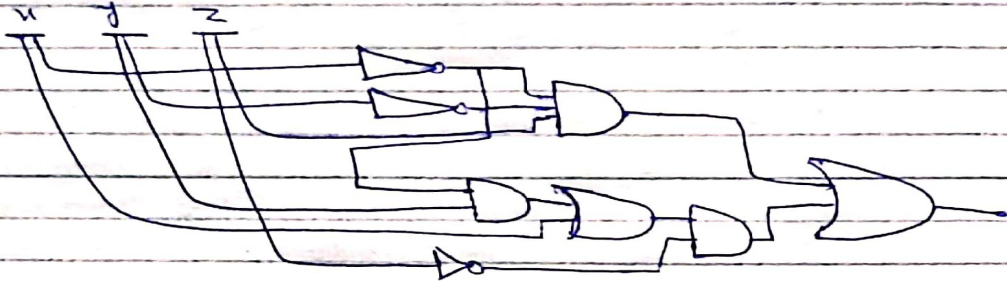

F<sub>8</sub>:
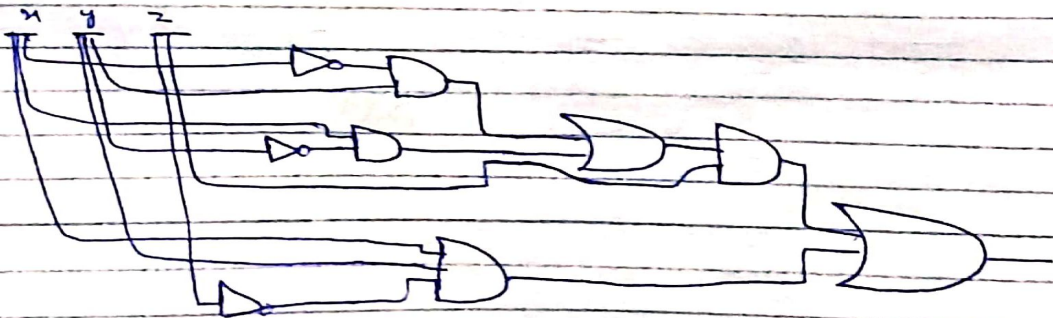
$$\begin{aligned}
 F_8(x, y, z) &= \sum m(3, 5, 6) \\
 &= (\bar{x}yz + x\bar{y}z + xy\bar{z}) \\
 F_8(x, y, z) &= z(\bar{x}y + x\bar{y}) + xy\bar{z}
 \end{aligned}$$





Page (2)

$x = \phi$   $y = \phi$   $z = \phi$

F<sub>9</sub>:

$$\begin{aligned} F_9(x, y, z) &= \sum m(1, 3, 5, 7) \\ &= (\bar{x}\bar{y}z + \bar{x}yz + x\bar{y}z + xyz) \\ &= \bar{x}\bar{y}z + x\bar{y}z + \bar{x}yz + xyz \\ &= z(\bar{x}\bar{y} + x\bar{y} + \bar{x}y + xy) \\ &= z + \bar{x}\bar{y}z + x\bar{y}z \\ &= z(1 + \bar{x}\bar{y} + x\bar{y}) \end{aligned}$$


As  $1 + \text{anything} = 1$  so

$$F_9(x, y, z) = z(1 + \bar{x}\bar{y})$$

again

$$\boxed{F_9(x, y, z) = z} \quad \text{So}$$

Circuit:

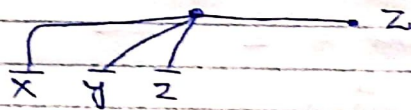

F<sub>10</sub>:

$$\begin{aligned} F_{10}(x, y, z) &= \sum m(4, 5, 7) \\ &= (x\bar{y}\bar{z} + x\bar{y}z + xyz) \\ &= x\bar{y}\bar{z} + x\bar{y}z + xyz \\ &= x(\bar{y}\bar{z} + \bar{y}z) + xyz \\ &= x(1) + x\bar{y}z \\ &= x(1 + \bar{y}z) \end{aligned}$$

As  $1 + \text{anything} = 1$  so

$$\boxed{F_{10}(x, y, z) = x}$$


Q NO 2)

W	X	Y	Z	F1	F2	max terms.
0	0	0	0	0	0	$W + X + Y + Z$ m0
0	0	0	1	0	0	$W + X + Y + Z'$ m1
0	0	1	0	0	1	$W + X + Y' + Z$ m2
0	0	1	1	1	1	$W + X + Y' + Z'$ m3
0	1	0	0	1	1	$W + X' + Y + Z$ m4
0	1	0	1	0	0	$W + X' + Y + Z'$ m5
0	1	1	0	0	0	$W + X' + Y' + Z$ m6
0	1	1	1	1	0	$W + X' + Y' + Z'$ m7
1	0	0	0	1	1	$W' + X + Y + Z$ m8
1	0	0	1	1	1	$W' + X + Y' + Z$ m9
1	0	1	0	0	0	$W' + X' + Y + Z$ m10
1	0	1	1	0	0	$W' + X' + Y' + Z$ m11
1	1	0	0	0	1	$W' + X' + Y' + Z'$ m12
1	1	0	1	1	1	$W' + X' + Y + Z'$ m13
1	1	1	0	1	0	$W' + X' + Y' + Z'$ m14
1	1	1	1	1	1	$W' + X' + Y' + Z'$ m15

$$F_1(W, x, y, z) = \overline{m_0} \cdot m_1 \cdot m_5 \cdot m_6$$

$$F_1(W, x, y, z) = (W + x + y + z) \cdot (W + x + y + z') \cdot (W + x' + y + z) \cdot (W + x' + y' + z)$$


Now Draw a circuit diagram:-

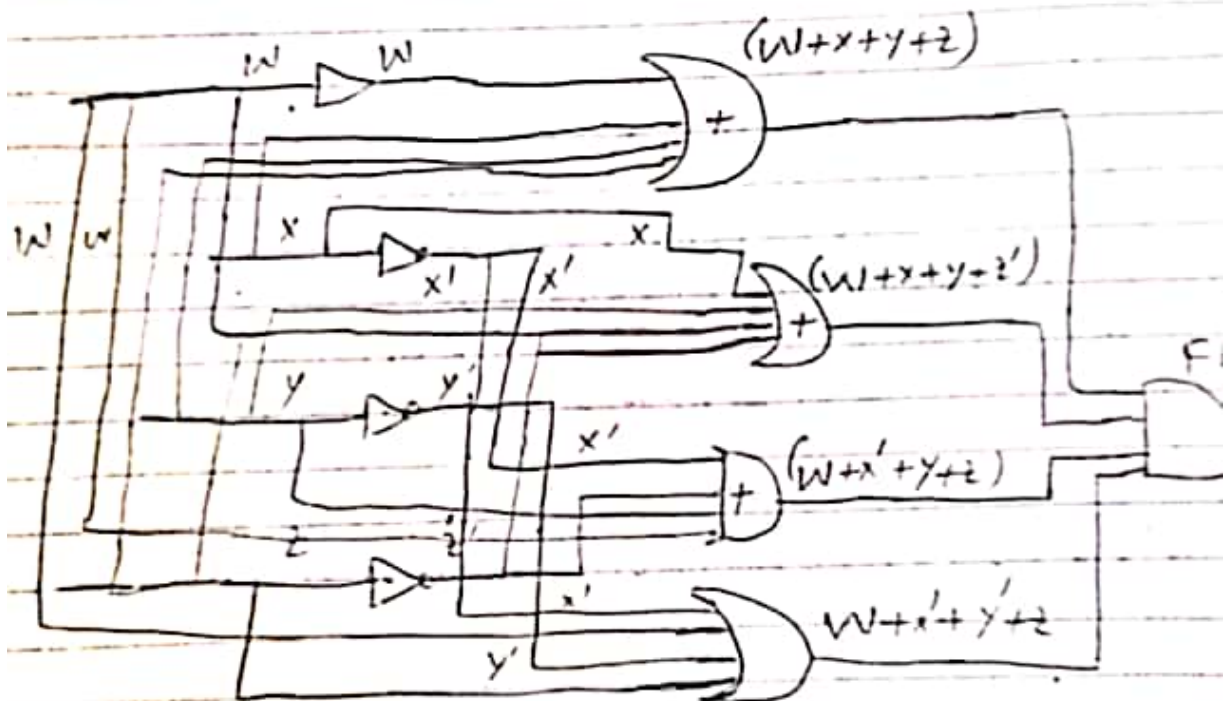

Function  $F_2$

$$F_2(W, x, y, z) = (A+B+C+D)(W+x+y+z)(W'+x+y'z)(W'+x'+y+z)$$

Draw a circuit diagram for  $F_3$

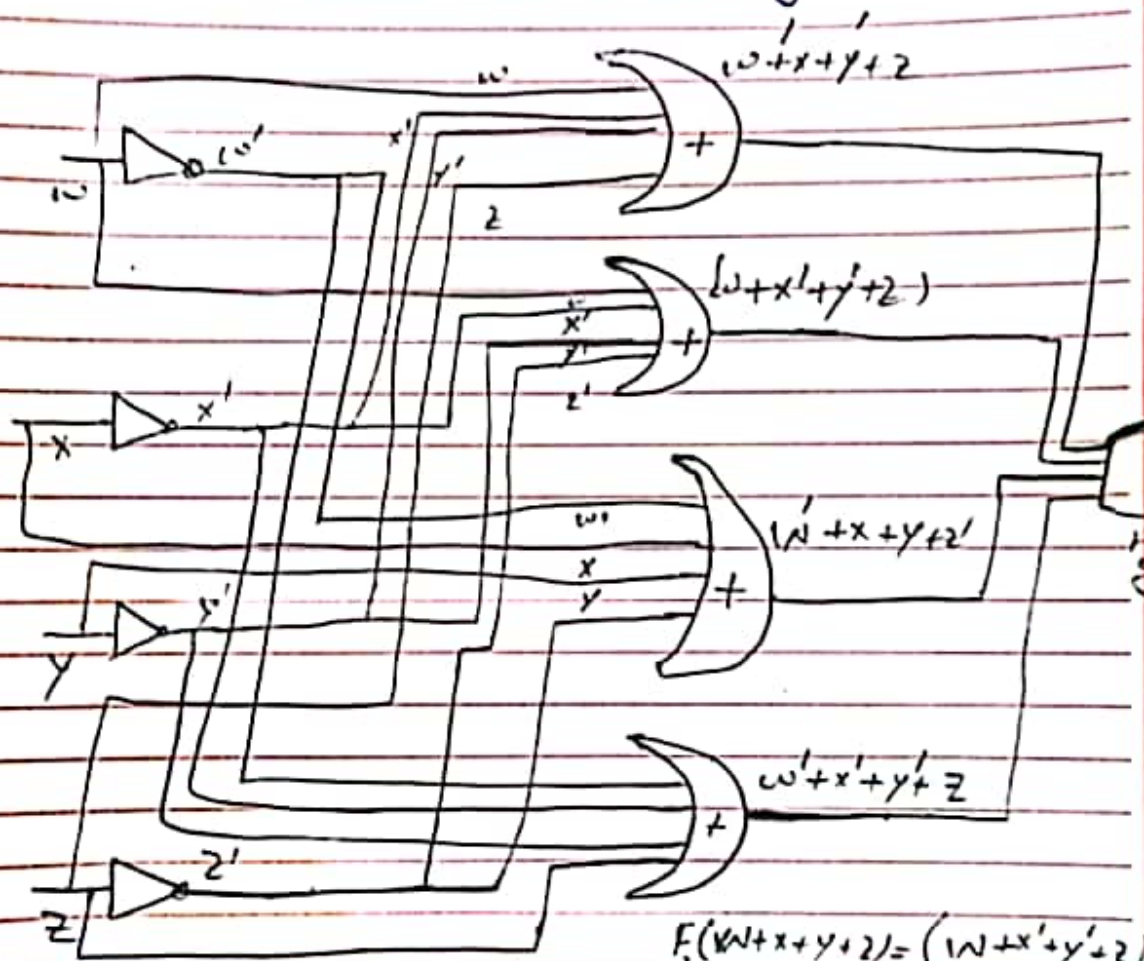

$$F_3(w+x+y+z) = (w+x'+y'+z) \cdot (w'+x'+y'+z') \cdot (w'+x+y+z')$$



$$F5(W, X, Y, Z) = (W + X' + Y' + Z)(W' + X + Y + Z)(W' + X + Y' + Z)(W' + X' + Y + Z)$$

Draw a circuit diagram F5

