

Circuits and Systems 1 - Week 6

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Ohm Law: $V = IR$

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Ohm Law: $V = IR$

KCL: Sum of current entering a node = sum of current leaving that node.

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Ohm Law: $V = IR$

KCL: Sum of current entering a node = sum of current leaving that node.

KVL: Algebraic sum of voltages in a loop is zero.

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Ohm Law: $V = IR$

KCL: Sum of current entering a node = sum of current leaving that node.

KVL: Algebraic sum of voltages in a loop is zero.

In this week inshaAllah, we will study two more techniques for circuit analysis.

Chapter 4 - Methods of Analysis of Resistive Circuits

Till now, we are familiar with 3 methods used in circuit analysis.

Ohm Law: $V = IR$

KCL: Sum of current entering a node = sum of current leaving that node.

KVL: Algebraic sum of voltages in a loop is zero.

In this week inshaAllah, we will study two more techniques for circuit analysis. **WHY?**

Chapter 4 - Methods of Analysis of Resistive Circuits

In simple maths, you need n equations for n unknowns. If the circuit elements increase, then the number of equations also increase.

Obtain the equations for current at node a in this circuit below.

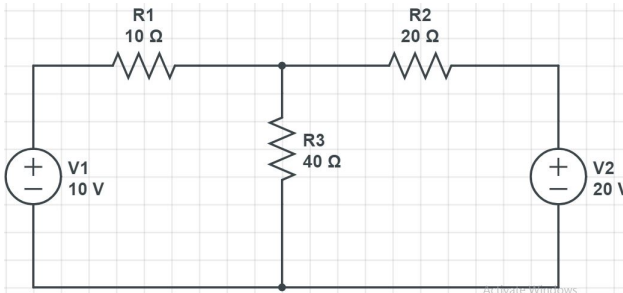


Figure: Example for motivation

Chapter 4 - Methods of Analysis of Resistive Circuits

When the number of circuit elements increases (or nodes or loops), the analysis using KCL and KVL become complex.

Two more/extra techniques which are used in combination with KCL and KVL.

- 1 Node voltage method or Nodal method
- 2 Mesh current method or Mesh method

Nodal Analysis

If there are n nodes in a circuit, so we label one node as [reference node](#) and write equations for the remaining $n - 1$ nodes.

Nodal Analysis

If there are n nodes in a circuit, so we label one node as [reference node](#) and write equations for the remaining $n - 1$ nodes.

Once again to recall: what happens at node? Is sum of current equals zero or sum of voltage?

Nodal Analysis

If there are n nodes in a circuit, so we label one node as [reference node](#) and write equations for the remaining $n - 1$ nodes.

Once again to recall: what happens at node? Is sum of current equals zero or sum of voltage?

So writing equations means applying KCL and writing equations for current.

Nodal Analysis Example 1

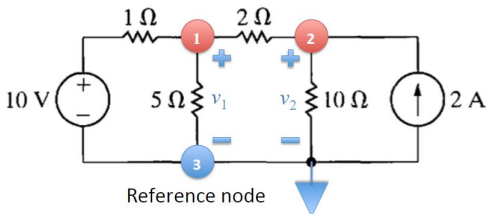


Figure: Example 1 using Nodal Analysis

At node 1:

$$\frac{10 - v_1}{1} = \frac{v_1 - v_2}{2} + \frac{v_1}{5} \quad (1)$$

At node 2:

$$\frac{v_1 - v_2}{2} + 2 = \frac{v_2}{10} \quad (2)$$

Nodal Analysis Example 2

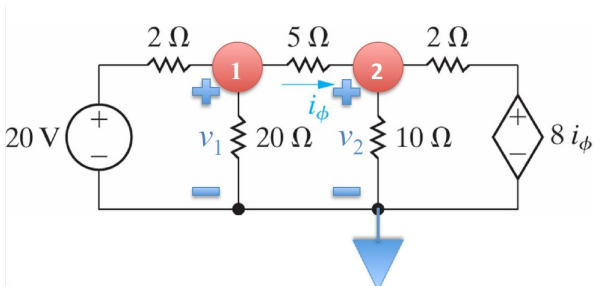


Figure: Example 2 using Nodal Analysis

Nodal Analysis Example 2

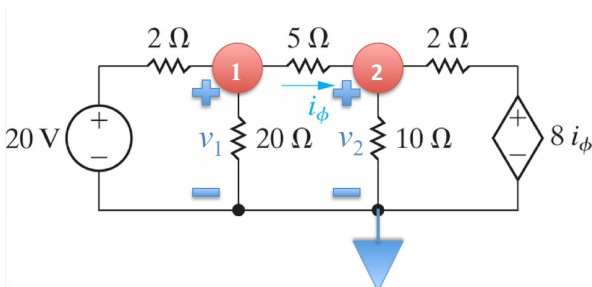


Figure: Example 2 using Nodal Analysis

$$\frac{v_1 - 20}{2} + \frac{v_1}{20} + \frac{v_1 - v_2}{5} = 0$$

$$\frac{v_1 - v_2}{5} = \frac{v_2}{10} + \frac{v_2 - 8i_\phi}{2}$$

$$i_\phi = \frac{v_1 - v_2}{5}$$

Nodal Analysis Tips

If we have n nodes, so we can write equations for $n - 1$ nodes.

Nodal Analysis Tips

If we have n nodes, so we can write equations for $n - 1$ nodes.

One node is called reference node or ground node (not actual ground but hypothetical ground).

Nodal Analysis Tips

If we have n nodes, so we can write equations for $n - 1$ nodes.

One node is called reference node or ground node (not actual ground but hypothetical ground).

Usually, we choose the bottom node as ground node.

Nodal Analysis Tips

If we have n nodes, so we can write equations for $n - 1$ nodes.

One node is called reference node or ground node (not actual ground but hypothetical ground).

Usually, we choose the bottom node as ground node.

Sometimes, we abuse notation by writing v_{ab} to actually denote $v_a - v_b$.

Nodal Analysis Tips

If we have n nodes, so we can write equations for $n - 1$ nodes.

One node is called reference node or ground node (not actual ground but hypothetical ground).

Usually, we choose the bottom node as ground node.

Sometimes, we abuse notation by writing v_{ab} to actually denote $v_a - v_b$.

Now lets proceed to the definition of **super node**.

Super Node

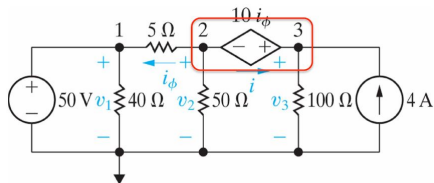


Figure: Example 3 - supernode concept

Obtain equations for node **2** and node **3**

Super Node

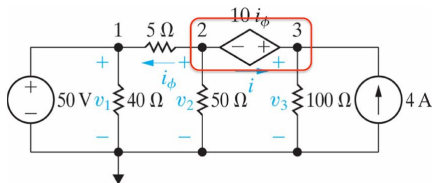


Figure: Example 3 - supernode concept

Obtain equations for node 2 and node 3

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + i = 0$$

$$i + 4 = \frac{v_3}{100}$$

$$i_\phi = \frac{v_2 - v_1}{5}$$

$$v_1 = v_1 - v_{\text{ref}} = 50$$

$$v_3 - v_2 = 10i_\phi$$

Super Node

Now $v_1 = 50$ is known and i can be eliminated

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + i = 0$$

$$i + 4 = \frac{v_3}{100}$$

We can write the following:

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0 \quad (3)$$

Super Node

Now $v_1 = 50$ is known and i can be eliminated

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + i = 0$$

$$i + 4 = \frac{v_3}{100}$$

We can write the following:

$$\frac{v_2 - v_1}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0 \quad (3)$$

Further we have the following 3 equations:

$$\frac{v_2 - 50}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0 \quad (4)$$

$$i_\phi = \frac{v_2 - 50}{5} \quad (5)$$

$$v_3 - v_2 = 10i_\phi \quad (6)$$

Super Node Example 4.3.2 page 120

Determine v_a and v_b in this circuit shown below

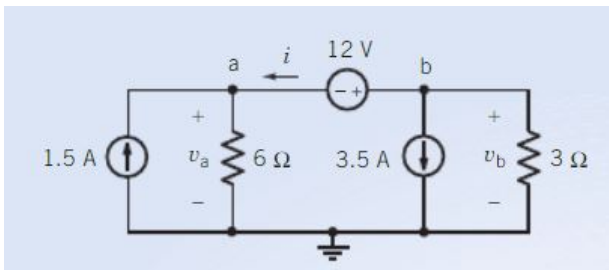


Figure: Example 4.3.2 on page 120 and 121

Super Node Example 4.3.2 page 120

KCL at node a:

$$1.5 + i = \frac{v_a}{6}$$

KCL at node b:

$$i + 3.5 + \frac{v_b}{3} = 0$$

Super node:

$$v_b - v_a = 12 \implies v_b = v_a + 12$$

Super Node Example 4.3.2 page 120

KCL at node a:

$$1.5 + i = \frac{v_a}{6}$$

KCL at node b:

$$i + 3.5 + \frac{v_b}{3} = 0$$

Super node:

$$v_b - v_a = 12 \implies v_b = v_a + 12$$

Substitute v_b in the above equation, we have the following 2 equations:

$$1.5 + i = \frac{v_a}{6}$$

$$i + 3.5 + \frac{v_a + 12}{3} = 0$$

Super Node Example 4.3.2 page 120

KCL at node a:

$$1.5 + i = \frac{v_a}{6}$$

KCL at node b:

$$i + 3.5 + \frac{v_b}{3} = 0$$

Super node:

$$v_b - v_a = 12 \implies v_b = v_a + 12$$

Substitute v_b in the above equation, we have the following 2 equations:

$$1.5 + i = \frac{v_a}{6}$$

$$i + 3.5 + \frac{v_a + 12}{3} = 0$$

Finally, we obtain $v_a = -12$ and $v_b = 0V$. Remember: Obtaining $0V$ is not an issue. If you can obtain negative voltages, then you can obtain $0V$ also - its zero voltage with reference to reference node.

Mesh Analysis Introduction

Mesh and loop are same terminologies.

Mesh Current Analysis involves obtaining equations in loops.

The important thing to consider is the direction of current flowing (and the direction of current opposing it).

Mesh Analysis Introduction

Mesh and loop are same terminologies.

Mesh Current Analysis involves obtaining equations in loops.

The important thing to consider is the direction of current flowing (and the direction of current opposing it).

Which circuit laws we apply in loops or meshes? KCL or KVL?

Mesh Analysis Introduction

Problem 4.5.1 on page 155

Mesh Analysis Introduction

Mesh 1 Equation:

$$4i_1 + 18(i_1 - i_3) + 6(i_1 - i_2) = 0$$

Mesh 2 Equation:

$$6(i_2 - i_1) + 12(i_2 - i_3) + 30 = 0$$

Mesh 3 Equation:

$$18(i_3 - i_1) + 12(i_3 - i_2) - 42 = 0$$

Mesh Analysis Introduction

Mesh 1 Equation:

$$4i_1 + 18(i_1 - i_3) + 6(i_1 - i_2) = 0$$

Mesh 2 Equation:

$$6(i_2 - i_1) + 12(i_2 - i_3) + 30 = 0$$

Mesh 3 Equation:

$$18(i_3 - i_1) + 12(i_3 - i_2) - 42 = 0$$

Now we have 3 equations and 3 unknowns. Further simplification gives us the following:

$$\begin{aligned} 28i_1 - 6i_2 - 18i_3 &= 0 \\ -6i_1 + 18i_2 - 12i_3 &= -30 \\ -18i_1 - 12i_2 + 30i_3 &= 42 \end{aligned} \tag{7}$$